

Feedback Transconductance Amplifier

N Yashodhan Reddy*

Consider a feedback transconductance amplifier as shown in the figure. It utilizes an op amp with open-loop gain μ , very large resistance, and an NMOS transistor Q . The amplifier delivers its output current to R_L . The feedback network, composed of resistor R , senses the equal current in the source terminal of Q and delivers a proportional voltage V_f to the negative input terminal of the op amp.

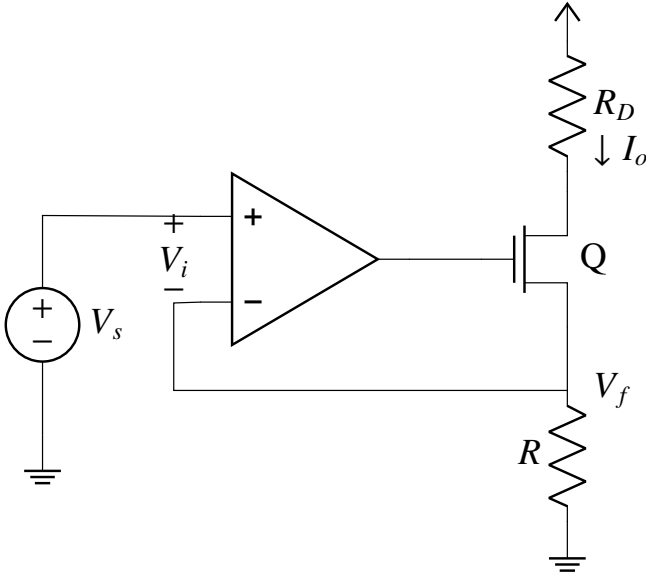


Fig. 0

1. Show that the feedback is negative.
2. Open the feedback loop by breaking the connection of R to the negative input of the op amp and grounding the negative input terminal. Find an expression for $A \equiv \frac{I_o}{V_i}$
3. Find an expression for $\beta \equiv \frac{V_f}{I_o}$
4. Find an expression for $A_f \equiv \frac{I_o}{V_s}$
5. What is the condition to obtain $I_o \approx \frac{V_s}{R}$

1. Show that the feedback is negative.

Solution: Suppose if source voltage V_s increases, then V_G increases
Since,

$$I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad (1.1)$$

$$I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_f - V_{TH})^2 \quad (1.2)$$

which thereby increases I_o

Now, since I_o is increasing,

$V_f (= I_o R)$ increases.

and V_f is feedback to negative terminal of the amplifier.

Hence, the system is in negative feedback.

2. Find an expression for $A \equiv \frac{I_o}{V_i}$

Solution: Applying small signal analysis, we get the resultant circuit as follows

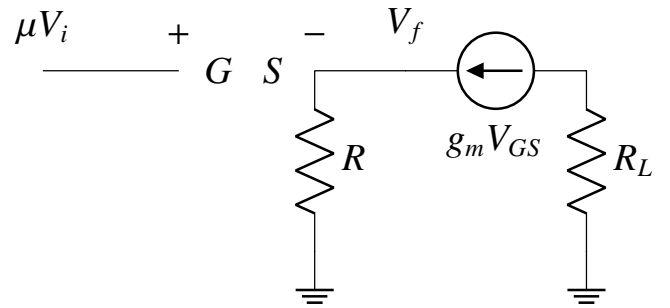


Fig. 2

$$V_f = I_o R \quad (2.1)$$

and

$$I_o = g_m (\mu V_i - V_f) \quad (2.2)$$

$$= g_m (\mu V_i - I_o R) \quad (2.3)$$

$$\Rightarrow (1 + g_m R) I_o = g_m \mu V_i \quad (2.4)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

Therefore,

$$A \equiv \frac{I_o}{V_i} = \frac{g_m \mu}{1 + g_m R} \quad (2.5)$$

3. Find an expression for $\beta \equiv \frac{V_f}{I_o}$

Solution: From the circuit diagram, Fig: 0

$$V_f = I_o R \quad (3.1)$$

Therefore,

$$\beta \equiv \frac{V_f}{I_o} = R \quad (3.2)$$

4. Find an expression for $A_f \equiv \frac{I_o}{V_s}$

Solution: Applying small signal analysis, we get the resultant circuit as follows

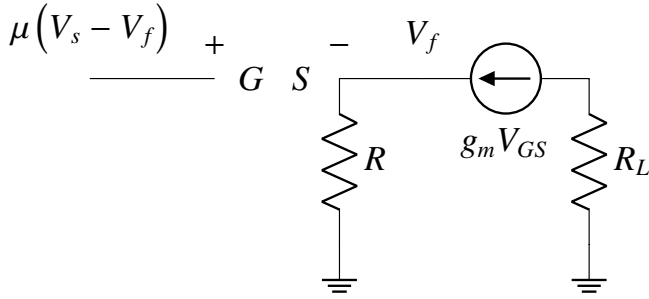


Fig. 4

$$I_o = g_m V_{gs} \quad (4.1)$$

$$= g_m (\mu (V_s - V_f) - V_f) \quad (4.2)$$

$$= g_m (\mu V_s - (\mu + 1) V_f) \quad (4.3)$$

$$= g_m \mu V_s - g_m (\mu + 1) I_o R \quad (4.4)$$

$$\Rightarrow (1 + g_m (\mu + 1) R) I_o = g_m \mu V_s \quad (4.5)$$

$$(4.6)$$

Therefore,

$$A_f \equiv \frac{I_o}{V_s} = \frac{g_m \mu}{1 + g_m (\mu + 1) R} \quad (4.7)$$

5. What is the condition to obtain $I_o \approx \frac{V_s}{R}$

Solution: From the circuit diagram, Fig: 0

$$I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad (5.1)$$

$$I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_f - V_{TH})^2 \quad (5.2)$$

and

$$V_f = I_o R \quad (5.3)$$

$$\Rightarrow I_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (\mu V_s - (\mu + 1) I_o R - V_{TH})^2 \quad (5.4)$$

If

$$I_o \ll \frac{\mu_n C_{ox} W}{2L} \quad (5.5)$$

and

$$\mu \gg 1 \quad (5.6)$$

From equation (5.4), we get

$$\sqrt{\frac{2I_o}{\mu_n C_{ox} \frac{W}{L}}} \ll \mu V_s - (\mu + 1) I_o R \quad (5.7)$$

$$(5.8)$$

then,

$$\mu V_s \approx (\mu + 1) I_o R - V_{TH} \quad (5.9)$$

which can be approximated to

$$V_s \approx I_o R \quad (5.10)$$

Thus, $\mu \gg 1$ and $I_o \ll \frac{\mu_n C_{ox} W}{2L}$ are the conditions to obtain $V_s \approx I_o R$